Computer Architecture – Introduction to Computer (計算機概論



Winston H. Hsu (徐宏民) National Taiwan University, Taipei


November 14, 2022

Office: R512, CSIE Building Communication and Multimedia Lab (通訊與多媒體實驗室) http://winstonhsu.info

The majority of the slides are from the chapter 5 in [Nisan and Schocken]


Babbage's Analytical Engine (1835)

 "We may say most aptly that the Analytical Engine weaves algebraic patterns just as the Jacquard-loom weaves flowers and leaves" 提花織布機 (Ada Lovelace)





Charles Babbage (1791-1871)

 


https://en.wikipedia.org/wiki/Analytical Engine


Some Early Computers and Computer Scientists




Blaise Pascal 1623-1662

 


Gottfried Leibniz 1646-1716

 


 

IC, Fall 2022 – Winston Hsu

Von Neumann Machine (around 1940)

 

 

Stored program concept!



John Von Neumann (and others) ... made it possible

Andy Grove (and others) ... made it small and fast.

Stored Program Concept


- Formulated independently by several mathematicians in the 1930s, the stored program concept is still considered the most profound invention in, if not the very foundation of, modern computer science.
- A scientific breakthrough
- The program's code is stored and manipulated in the computer memory, just like data, becoming what is known as "software."

IC, Fall 2022 – Winston Hsu

Turing Machine vs. von Neumann Machine

- The Turing machine an abstract artifact describing a deceptively simple computer – is used mainly to analyze the logical foundations
- In contrast, the von Neumann machine is a practical architecture and the conceptual blueprint of almost all computer platforms today.

Processing Logic: Fetch-Execute Cycle

 


- Executing the current instruction involves one or more of the following micro-tasks:
 - Have the ALU compute some function out = f (register values)
 - Write the ALU output to selected registers
 - As a side-effect of this computation, figure out which instruction to fetch and execute next.


IC, Fall 2022 – Winston Hsu

The CPU-Memory Gap (1/2)

 
The increasing gap between DRAM, disk, and CPU speeds.



The CPU-Memory Gap (2/2)

 


IC, Fall 2022 – Winston Hsu

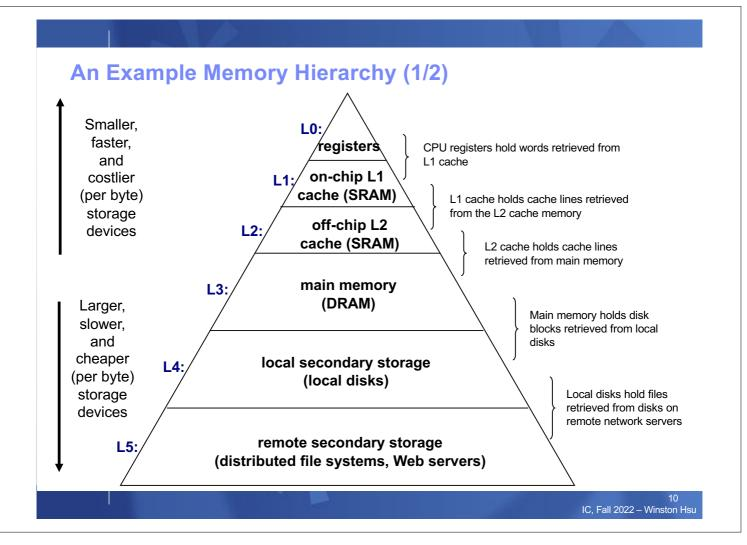

An Example Memory Hierarchy (2/2)

 Take the numbers as relative measures; outdated.



IC, Fall 2022 – Winston Hsu

The "Hack" Chip-Set and Hardware Platform

Elementary logic gates

- Nand
- Not
- And
- Or
- Xor
- Mux
- Dmux
- Not16
- And16
- Or16
- Mux16
- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

Combinational chips

- HalfAdder
- FullAdder
- Add16
- Inc16
- ALU

Sequential chips

- DFF
- Bit
- Register
- RAM8
- RAM64
- RAM512
- RAM4K
- RAM16K
- PC

Computer Architecture

- Memory
- CPU
- Computer



The "Hack" Computer (Example)

- A 16-bit Von Neumann platform
- The instruction memory and the data memory are physically separate
- Screen: 256 rows by 512 columns, black and white
- Keyboard: standard
- Designed to execute programs written in the Hack machine language
- Can be easily built from the chip-set that we built so far in the course

Main parts of the Hack computer:

- Instruction memory (ROM)
- Memory (RAM):
 - Data memory
 - Screen (memory map)
 - Keyboard (memory map)



reset Computer

Why OS?

Computer (the logic that holds everything together).

IC, Fall 2022 – Winston Hsu


Lecture / construction plan



Instruction memory

- Memory:
 - Data memory
 - □ Screen
 - Keyboard
- **CPU**
- Computer

Instruction Memory

 

Function:

- The ROM is pre-loaded with a program written in the Hack machine language
- The ROM chip always emits a 16-bit number:

• This number is interpreted as the *current instruction*.

15 IC, Fall 2022 – Winston Hsu


Data Memory

Low-level (hardware) read/write logic:

To read RAM[k]: set address to k, probe out

To write RAM[k]=x: set address to k, set in to x, set load to 1,

run the clock

 

High-level (OS) read/write logic:

To read RAM[k]: use the OS command out = peek(k)


To write RAM[k]=x: use the OS command poke(k,x)

peek and poke are OS commands whose implementation should effect the same behavior as the low-level commands (in the sample computer)

Register file implementation

Implementation example: TOY main memory.

 
- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



Memory Array

Wordline:

 - like an enable
- single row in memory array read/written
- corresponds to unique address
- only one wordline HIGH at once



18

Lecture / construction plan

- Instruction memory
- Memory:
 - Data memory
 - Screen
 - Keyboard
 - CPU
 - Computer

19 IC, Fall 2022 – Winston Hsu


Memory: conceptual / programmer's view

Data Screen memory map Keyboard map Keyboard

Using the memory:

- □ To record or recall values (e.g. variables, objects, arrays), use the first 16K words of the memory
- □ To write to the screen (or read the screen), use the next 8K words of the memory
- □ To read which key is currently pressed, use the next word of the memory.

Memory: physical implementation

 

- □ Access to any address from 0 to 16,383 results in accessing the RAM16K chip-part
- □ Access to any address from 16,384 to 24,575 results in accessing the Screen chip-part
- □ Access to address 24,576 results in accessing the keyboard chip-part
- Access to any other address is invalid.

21 IC, Fall 2022 – Winston Hsu

The Memory chip is essentially a


Lecture / construction plan

- Instruction memory
- Memory:
 - Data memory



- Screen
- Keyboard
- CPU
- Computer

Screen

 

The Screen chip has a basic RAM chip functionality:

- ☐ read logic: out = Screen[address]
- ☐ write logic: if load then Screen[address] = in


Side effect:


Continuously refreshes a 256 by 512 black-and-white screen device

23 IC, Fall 2022 – Winston Hsu

Screen Memory Map

 In the Hack platform, the screen is implemented as an 8K 16-bit RAM chip.



 

How to set the (row, col) pixel of the screen to black or to white:

- □ Low-level (machine language): Set the col%16 bit of the word found at Screen[row*32+col/16] to 1 or to 0 (col/16 is integer division)
- □ High-level: Use the OS command drawPixel(row,col)

 (effects the same operation, discussed later in the course, when we'll write the OS).

Keyboard



Keyboard chip: a single 16-bit register

Input: scan-code (16-bit value) of the currently

pressed key, or 0 if no key is pressed

Output: same

Special keys:

Key pressed	Keyboard output	Key pressed	Keyboard output			
newline	128	end	135			
backspace	129	page up	136			
left arrow	130	page down	137			
up arrow	131	insert	138			
right arrow	132	delete	139			
down arrow	133	esc	140			
home	134	f1-f12	141-152			

- Synchronous vs. Asynchronous
- Signal

- How to read the keyboard:
- □ Low-level (hardware): probe the contents of the Keyboard chip
- □ High-level: use the OS command keyPressed() (effects the same operation, discussed later in the course, when we'll write the OS).

25


IC, Fall 2022 – Winston Hsu

Lecture / construction plan

- Instruction memory
- Memory:
 - Data memory
 - □ Screen
 - Keyboard



Computer

 


CPU internal components (invisible in this chip diagram): ALU and 3 registers: A, D, PC

CPU execute logic:

The CPU executes the instruction according to the Hack language specification:

- ☐ The D and A values, if they appear in the instruction, are read from (or written to) the respective CPU-resident registers
- ☐ The M value, if there is one in the instruction's RHS, is read from inM
- □ If the instruction's LHS includes M, then the ALU output is placed in outM, the value of the CPU-resident A register is placed in addressM, and writeM is asserted.

27 IC, Fall 2022 – Winston Hsu

 

CPU internal components (invisible in this chip diagram): ALU and 3 registers: A, D, PC

CPU fetch logic:

Recall that:

- 1. the instruction may include a jump directive (expressed as non-zero jump bits)
- 2. the ALU emits two control bits, indicating if the ALU output is zero or less than zero

If reset==0: the CPU uses this information (the jump bits and the ALU control bits) as follows:

If there should be a jump, the PC is set to the value of A; else, PC is set to PC+1

If reset==1: the PC is set to 0. (restarting the computer)

The C-instruction

dest = comp; jump					comp							dest jump)
Γ													- 1	1		
binary:	1	1	1	a	c1	c2	с3	c 4	c5	с6	d1	d2	d3	j 1	j2	ј3

(when a=0)	l .						(when a=1)	d1	d2	d3	Mnemonic	Destination	ı (where to sto	re the computed value)			
comp	c1	c2	с3	c4	c5	c6	comp	0	0	0	null	The value i	value is not stored anywhere				
0	1	0	1	0	1	0		0	O 0 1 M Memory[A] (memory register addressed by					ister addressed by A)			
1	1	1	1	1	1	1		0	1	0	D	D register					
-1	1	1	1	0	1	0		0	1	1	MD	Memory[A] and D register					
D	0	0	1	1	0	0											
A	1	1	0	0	0	0	м	1	1 0 0 A Aregister								
!D	0	0	1	1	0	1		1 0 1 AM A register and Memory[A]						.]			
! A	1	1	0	0	0	1	! M	1	1	0	AD	A register and D register					
-D	0	0	1	1	1	1		1	1	1	AMD	A register, Memory[A], and D register					
-A	1	1	0	0	1	1	-M				I			-			
D+1	0	1	1	1	1	1			j1		j2	j3	Mnemonic	Effect			
À+1	1	1	0	1	1	1	M+1	(out < 0)		(0)	(out = 0)	(out > 0)	Willelifollic				
D-1	0	0	1	1	1	0			0		0	0	null	No jump			
A-1	1	1	0	0	1	0	M-1		0		0	1	JGT	If $out > 0$ jump			
D+A	0	0	0	0	1	0	D+M		0		1	0	JEQ	If $out = 0$ jump			
D-A	0	1	0	0	1	1	D-M		0		1	1	JGE	If <i>out</i> ≥0 jump			
A-D	0	0	0	1	1	1	M-D		1		0	0	JLT	If out <0 jump			
DeA	0	0	0	0	0	0	DeM		1		0	1	JNE	If <i>out</i> ≠ 0 jump			
DIA	0	1	0	1	0	1	DIM		1		1	0	JLE	If out ≤0 jump			
DIN		_				-		L	1		1	1	JMP	Jump			

IC, Fall 2022 – Winston Hsu

IC, Fall 2022 – Winston Hsu

dest = comp; jumpdest **CPU** implementation **1 1 1** a c1 c2 c3 c4 c5 c6 d1 d2 d3 j1 j2 j3 Chip diagram: □ Includes most of the ALU output CPU's execution logic □ The CPU's control logic is hinted: each circled "c" (c) represents one or more control bits, taken from the instruction (c) decode outM □ The "decode" ALU bar does not **▶**(C) represent a instruction A/M chip, but rather indicates inM that the (c)writeM instruction bits are decoded ▶ addressM somehow. reset Cycle: **Execute logic:** Fetch logic: Resetting the computer: ■ Execute If there should be a jump, Set reset to 1, Decode set PC to A then set it to 0. □ Fetch

else set PC to PC+1

Execute


Lecture / Construction plan

- Instruction memory
- Memory:
 - Data memory
 - Screen
 - Keyboard
- CPU



31 IC, Fall 2022 – Winston Hsu

Computer-on-a-chip interface

 

Chip Name: Computer // Topmost chip in the Hack platform

Input: reset

Function: When reset is 0, the program stored in the

computer's ROM executes. When reset is 1, the execution of the program restarts. Thus, to start a program's execution, reset must be pushed "up" (1)

and "down" (0).

From this point onward the user is at the mercy of the software. In particular, depending on the program's code, the screen may show some output and the user may be able to interact with the computer

via the keyboard.

Perspective: from Here to a "Real" Computer

- Caching
- More I/O units
- Special-purpose processors (I/O, graphics, GPU, communications, ...)
- Multi-core / parallelism
- Efficiency
- Energy consumption considerations
- And more ...

33 IC, Fall 2022 – Winston Hsu

Perspective: Some Issues we haven't Discussed (among many)

- CISC / RISC (hardware / software trade-off)
 - complex instruction set computer vs. reduced instruction set computer
- Hardware diversity: desktop, laptop, hand-held, game machines, ...
- General-purpose vs. embedded computers
- Silicon compilers
- And more ...

CISC vs. RISC

CISC

- Emphasis on hardware
- Multiple instruction sizes and formats
- Less registers
- More addressing modes
- Extensive use of microprogramming
- Instructions take a varying amount of cycle time
- Pipeline is difficult

RISC

- Emphasis on software
- Instructions of same set with few formats
- Use more registers
- Few addressing modes
- Complexity in computer
- Instructions take one cycle time
- Pipeline is easy



35 IC, Fall 2022 – Winston Hsu